

Chapter 3


Delay

關志達

台灣大學電機系

Delay in Circuits


- **Propagation delay** time, t_{pd} = **maximum** time between input transition (50%) to output crossing 50% output level.
 - t_{pdf} , t_{pdr}
- **Contamination delay** time, t_{cd} = **minimum** time between input transition (50%) to output crossing 50% output level.
- When a signal travels with contamination delay and violate hold time of the following FF, the output value may be "contaminated" by the faster-than-normal signal. This condition is called "**race**."

 

Transition Times

- **Rise time**, t_r = time for a waveform to rise from 20% to 80% of its steady-state value.
- **Fall time**, t_f = time for a waveform to fall from 80% to 20% of its steady-state value.
- Average transition time,

$$t_{rf} = (t_r + t_f)/2$$

 





Gate RC Delay Estimation

- Delay of a gate is inversely proportional to its driving strength ($1/R$) and proportional to its load capacitance (C).
- Note that we can assume PMOS needs be **twice** as wide as NMOS to get same driving strength. Assume $\mu_n = 2\mu_p$
- Resistor
 - ON transistor can be modeled as a resistor.
- Capacitance
 - Gate capacitance
 - Diffusion capacitance
 - Wire capacitance


RC Analysis Example

W: transistor width

All transistors have same L

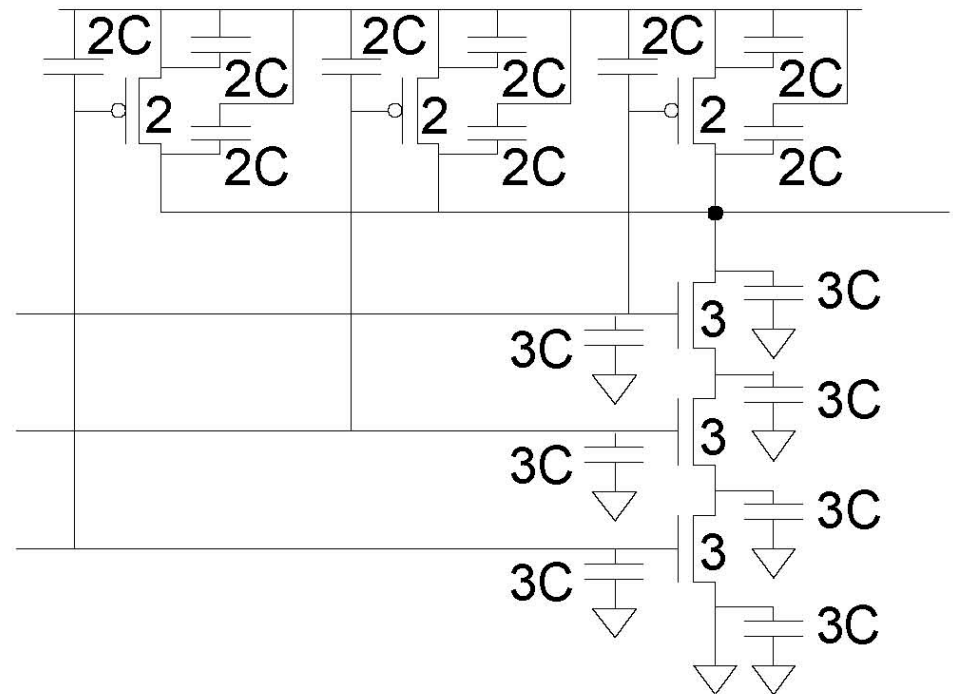 

Equivalent Circuit with RC

 


Treat Vdd as AC GND

Elmore Delay Model

- Pull-up and pull-down network are like RC ladder
- R is on the **shared path** from the **source** to the **node** and the **leaf** (the node to compute delay).


$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$




Elmore Delay Model Examples

■ Compute V_{out3}

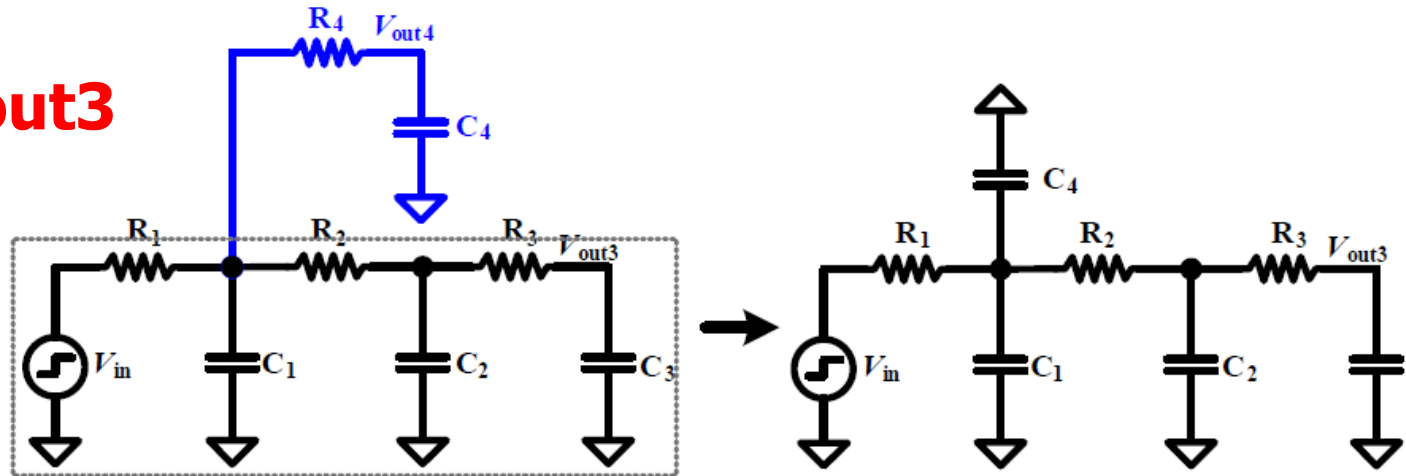


■ Compute V_{out4}

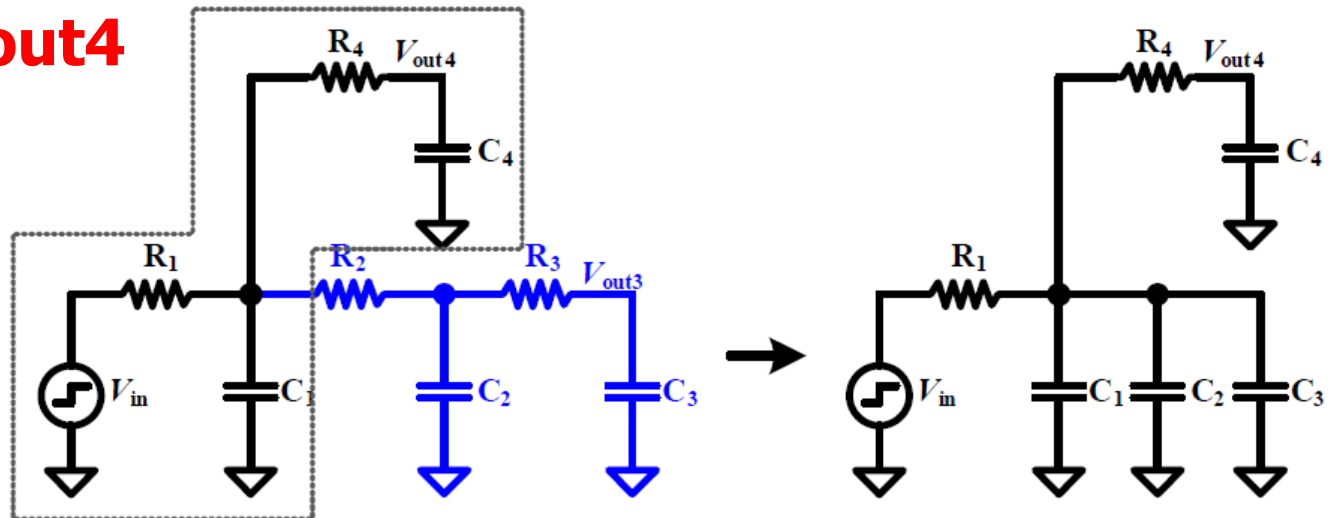

Delay Analysis Example



- 3-input NAND, no load

When Y goes LOW

 

$$\begin{aligned} t_{pdf} &= R(9C) + (2R/3)(3C) + (R/3)(3C) \\ &= \underline{12RC} \end{aligned}$$


When Y goes HIGH

  


$$\begin{aligned} t_{pdr} &= R(9C) + R(3C) + R(3C) \\ &= \underline{15RC} \end{aligned}$$

Loaded Analysis

 - h is the number of fanout 3-input NAND gates


 
$$\begin{aligned}
 t_{pdf} &= R(9C + 5hC) + (2R/3)(3C) + (R/3)(3C) \\
 &= \underline{(12 + 5h)RC}
 \end{aligned}$$



$$\begin{aligned}
 t_{pdr} &= R(9C + 5hC) + R(3C) + R(3C) \\
 &= \underline{(15 + 5h)RC}
 \end{aligned}$$


Linear Delay Model

- A common delay estimation approach in IC design is to treat logic gates as simple delay elements with the following delay time

$$t_{pd} = t_{internal} + t_{LE} * h$$

where $t_{internal}$ is the fixed parasitic internal delay and t_{LE} is the unit-output-loading logical effort delay; h is the number of fanout gates of the same type.
 
$$\begin{aligned} p &= t_{internal} \\ g &= t_{LE} \\ d &= t_{pd} \end{aligned}$$






Parasitic Delay ($t_{internal}$)


- Delay when the output load is zero. Can be obtained by simulation.
- Approximate formula says that the parasitic delay is proportional to N , the number of inputs in NAND/NOR gates.
- In practice, this is not true if we use a more accurate Elmore delay model. In this case, the parasitic delay grows with N^2 .
- It is not advisable to use more than 4-5 NMOS/PMOS series transistors.
- NMOS in series is always preferred to PMOS in series.

Logical Effort (g or t_{LE})

 
- The ratio of the input capacitance between the current gate and the inverter that can deliver the same output current level.
- Examples (all with unit resistance)



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

 

$$C_{in} = 7$$
$$g = 7/3$$



Input Waveform Slope

- The largest source of error in the linear model is the slope of the input waveform.
- The delay time formulas can be modified


$$t_{pd} = t_{pd-step} + t_{edge} * k$$

where $t_{pd-step}$ is the propagation delay assuming step input and t_{edge} is the input rise/fall time.

- Other sources of error in linear delay model include different input arrival times and parasitic capacitance C_{gs} and C_{gd} , and **wire capacitance**.

Stage Ratio

 - Very often, large drivers are needed to transmit signals over a long bus or a large load (e.g., output pads and bus driver). This is often achieved by a chain of successively large inverters.



Stage Ratio (cont'd)

- The optimal stage ratio (in the sense of least delay) satisfies the equation: $p_{inv} + \rho(1 - \ln \rho) = 0$, where p_{inv} is the parasitic delay and ρ is the stage ratio.
- The optimal is around 3.59 if $p_{inv} = 1$. For convenience 4 is often used. Actually any ρ between 2.4 and 6 gives a delay that is within 15% of the optimal value.

