



臺灣大學

# IC Design HW3 Tutorial

Hao-Yu Lan  
Professor : Tzi-Dar Chiueh  
2016/11/25



臺灣大學

# Outline

- Introduction to Verilog
  - Module
  - Value & number
  - Data type
- Verilog-XL simulation & nWave tool



臺灣大學

# Introduction to Verilog

Module  
Value & Number  
Data Type



臺灣大學


# What is Verilog

- Verilog is a Hardware Description Language (HDL)
  - Describe digital electronic system at multiple levels of abstraction
  - Model the timing
  - Express the *concurrency* of the system operation
  - Test the system



臺灣大學

# Behavioral Model of Circuits

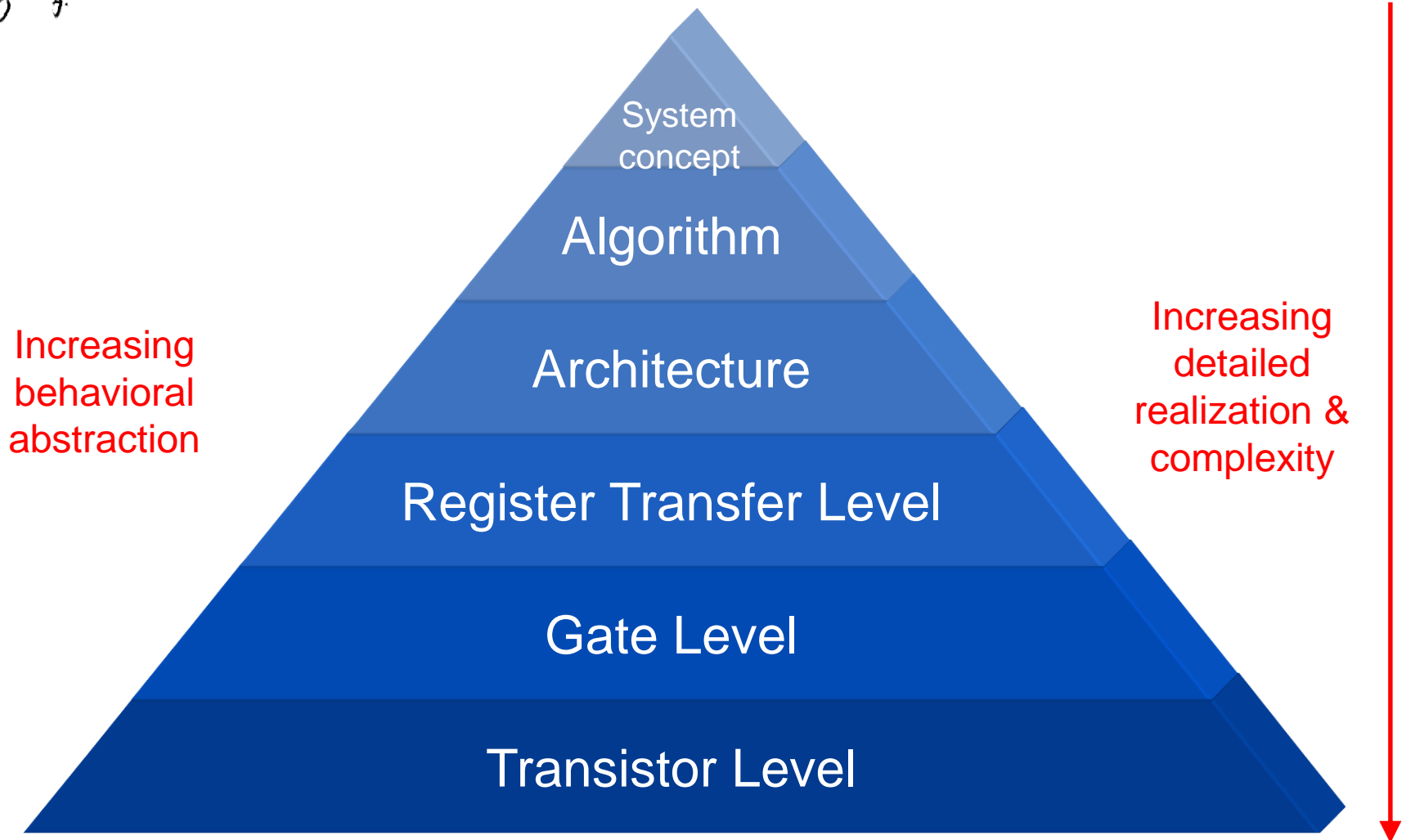



臺灣大學

# Verilog-Supported Levels of Abstraction

- Behavioral
  - Structural and procedural like the C programming language
  - Describe algorithm level and RTL level Verilog models
- Register Transfer Level (RTL)
  - Describe the flow of data between registers and how a design process these data.
- Structural
  - Describe gate-level and switch-level circuits.

High




Low



臺灣大學
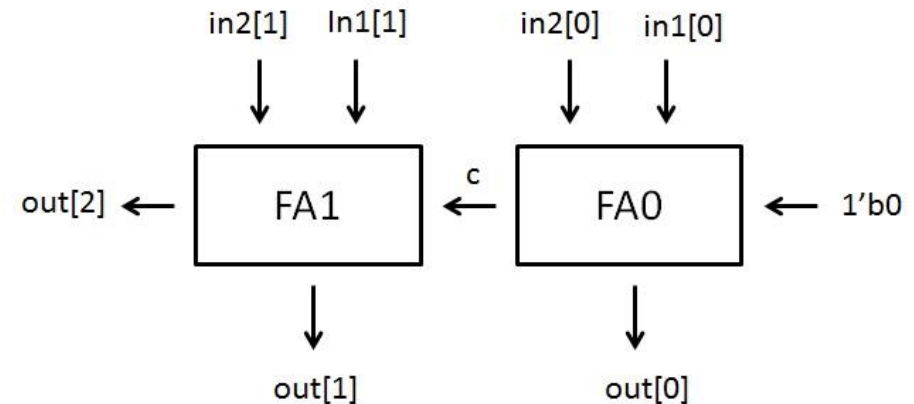
# The Verilog Module


- Basic building blocks .
- Begin with **module**,  
end with **endmodule**



```
module <module name>(<port lists>);
```

```
//module description
```

```
endmodule
```

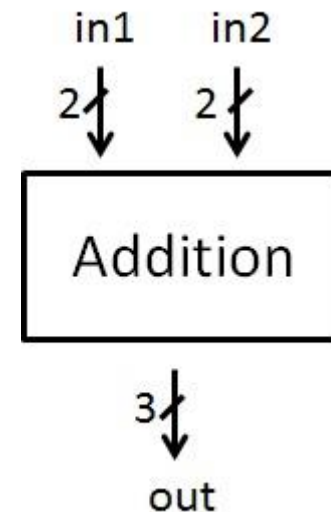




臺灣大學
 
# Module Ports

- Modules communicate through ports
  - input
  - output
  - inout (bidirectional)



```
module FD2 (Q, D, CLK, RESET);  
  
    output        Q;  
    input         CLK, D, RESET;  
  
    //module description  
  
endmodule
```





臺灣大學

# 4-Value Logic System

- 0
  - zero, false, low
- 1
  - one, true, high
- Z
  - high impedance, floating
- X
  - unknown, occurs at un-initialized storage elements or un-resolvable logic conflicts



臺灣大學

# Value and Number

- `[[<size>]'<radix>]<value>`
  - Size
    - The size in bits
    - Default size is 32 bits
  - Radix
    - b (binary), o (octal), d (decimal), h (hexadecimal)
    - Default radix is decimal
  - Value
    - Any legal number in selected radix, including “x” and “z”
- Radix and value are case-insensitive



臺灣大學

# Value and Number - Examples

`4'b1001` // 4-bit binary  
`5'D3` // 5-bit decimal  
`12'h7ff` // 12-bit hexadecimal  
`3'bx10` // 3-bit binary with unknown MSB  
`4'b101x` // 4-bit binary with unknown LSB  
`12'hx` // 12-bit unknown  
`-8'd6` // phrase as `-(8'd6)`

- underline usage
  - `16'b0001_0101_0001_1111`
  - `32'h12ab_f001`
- X and Z is sign-extended
  - Ex. 12-bit a
    - `a = 'h x; // yields xxx`
    - `a = 'h 3x; // yields 03x`
    - `a = 'h 0x; // yields 00x`



臺灣大學

# Data Type Classes

- **wire**
  - **wire** [MSB:LSB] *variables*;
  - input, inout, output are default to be wire.
  - Used to describe combinational circuit!
- **reg**
  - **reg** [MSB:LSB] *variables*
  - Used to describe combinational or sequential circuit.



臺灣大學

# Assign a value to wire


- wire
  - “assign “  
wire a;  
assign a = 1'b1;
  - Output port  
wire a;  
wire b;  
assign b = 1'b0;  
NOT n0(a, b);
- Every wire can be only assigned once!!!  
wire a;  
wire b;  
assign b = 1'b0;  
NOT n0(a, b);  
assign a = 1'b0; //Wrong!!!



臺灣大學
 
# Module Instances (1/2)

- Create a higher-level system by connecting lower-level components



```
module Reg2 (q, d, clk, rst);  
    output    [1:0] q;  
    input     [1:0] d;  
    input     clk, rst;  
    FD2 f0(q[0], d[0], clk, rst);  
    FD2 f1(.Q(q[1]), .D(d[1]),  
           .CLK(clk), .RESET(rst));  
endmodule
```


Module name

Instance name



臺灣大學

# Module Instances (2/2)

 

```
module Reg2_2 (q, d, clk, rst);

    output      [1:0] q;
    input       [1:0] d;
    input       clk, rst;

    wire        [1:0] w;

    Reg2 r0(w, d, clk, rst);
    Reg2 r1(q, w, clk, rst);

endmodule
```



臺灣大學

# Net Concatenations

Representation	Meaning
$\{b[3:0], c[2:0]\}$	$\{b[3], b[2], b[1], b[0], c[2], c[1], c[0]\}$
$\{a, b[3:0], w, 3'b101\}$	$\{a, b[3], b[2], b[1], b[0], w, 1'b1, 1'b0, 1'b1\}$
$\{4\{w\}\}$	$\{w, w, w, w\}$
$\{b, \{3\{a, b\}\}\}$	$\{b, a, b, a, b, a, b\}$





# Standard Cell Library (lib.v)

臺灣大學

- Choose what you need
- Compose your circuit according to I/O connections

```
module AN3(Z,A,B,C);
```

```
    output Z;  
    input A,B,C;
```

```
    // netlist
```

```
    and g1(Z,A,B,C);
```

```
    // specify block, declare local
```

```
    // timing constant
```

```
    specify
```

```
        // delay parameters
```

```
        specparam Tp_A_Z = 0.275;
```

```
        specparam Tp_B_Z = 0.275;
```

```
        specparam Tp_C_Z = 0.275;
```

```
        // path delay (full connection)
```

```
        ( A *> Z ) = ( Tp_A_Z );
```

```
        ( B *> Z ) = ( Tp_B_Z );
```

```
        ( C *> Z ) = ( Tp_C_Z );
```

```
    endspecify
```

```
endmodule
```



# Standard Cell Library (lib.v) - 2/2

臺灣大學

- IV // not
- AN3
- AN4
- AN2
- EN // xnor
- EN3
- EO // xor
- EO3
- FA1 // full adder
- FD1 // DFF
- FD2
- ND2 // nand
- ND3
- ND4
- NR2 // nor
- NR3
- OR2 // or
- OR3
- OR4
- HA1 // half adder
- MUX21H // 2-to-1 MUX



臺灣大學

# Notification

- In this HW, all the logic operation **MUST** consist of standard cell. You can **NOT** use logic operators.

~~wire a, b, c;  
assign a = b & c;~~


wire a, b, c;  
AN2 an(a, b, c);



臺灣大學
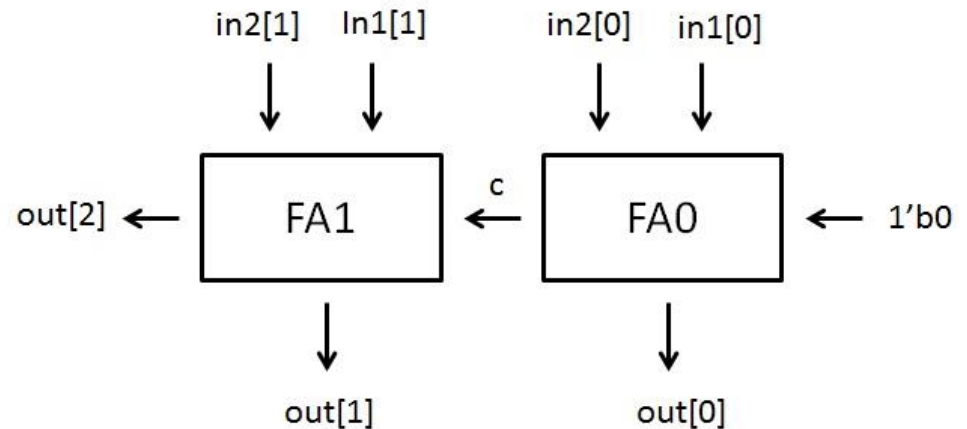
# Example

```
module ADDER (out, in1, in2);  
    output [2:0] out;  
    input [1:0] in1, in2;  
    wire c;
```




```
    FA1 fa0(c, out[0], in1[0], in2[0], 1'b0);  
    FA1 fa1(out[2], out[1], in1[1], in2[1], c);  
endmodule
```



臺灣大學

# Flow chart

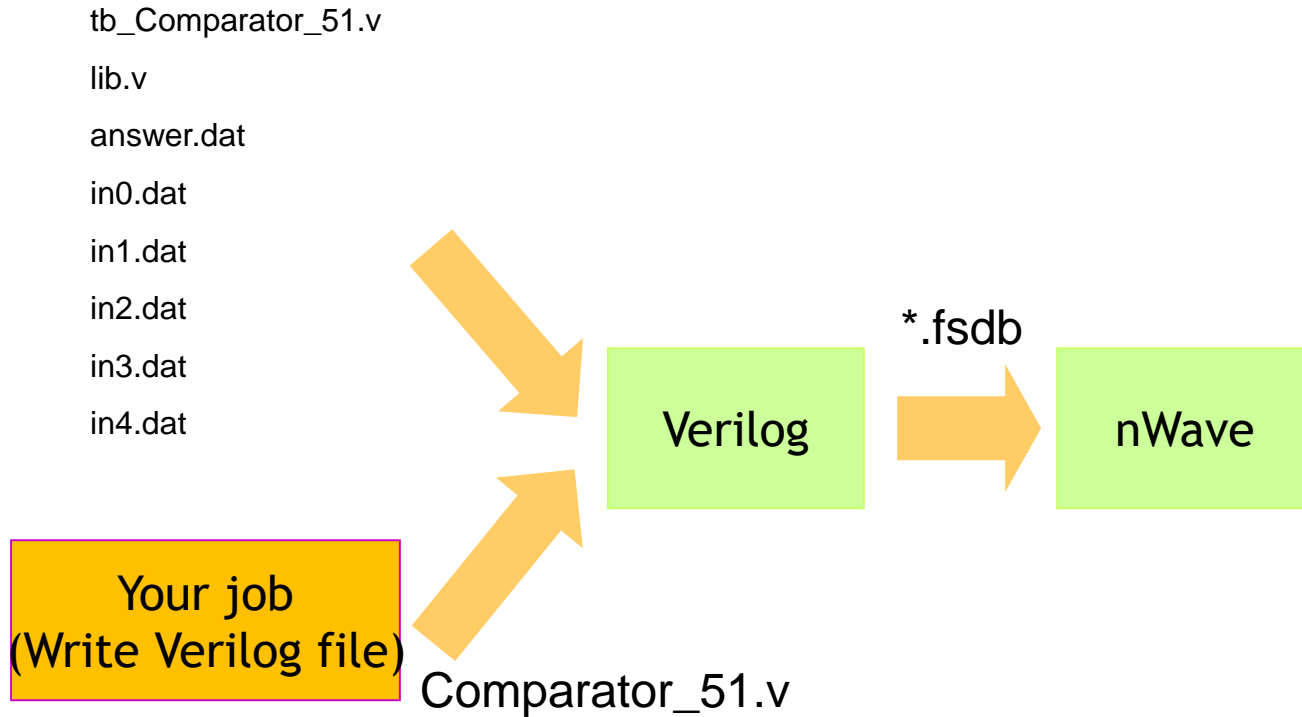


All these files should be placed under the same folder



臺灣大學

# Your Job

 

```
module COMPARATOR_51(median,  
i0, i1, i2, i3, i4);
```

```
output      [2:0] median;
```

```
input       [5:0] i0, i1, i2, i3, i4;
```

```
\\ Write your design here
```

```
wire        [?:0] ...;
```

```
My_module_0 M0(?, ?, ... , ?);
```

```
.....
```

```
My_module_x Mx(?, ?, ... , ?);
```

```
endmodule
```



臺灣大學

# Verilog-XL Simulation & nWave Tool




臺灣大學

# Test and verification your circuit

- By applying input patterns and observing output responses

## Testbench

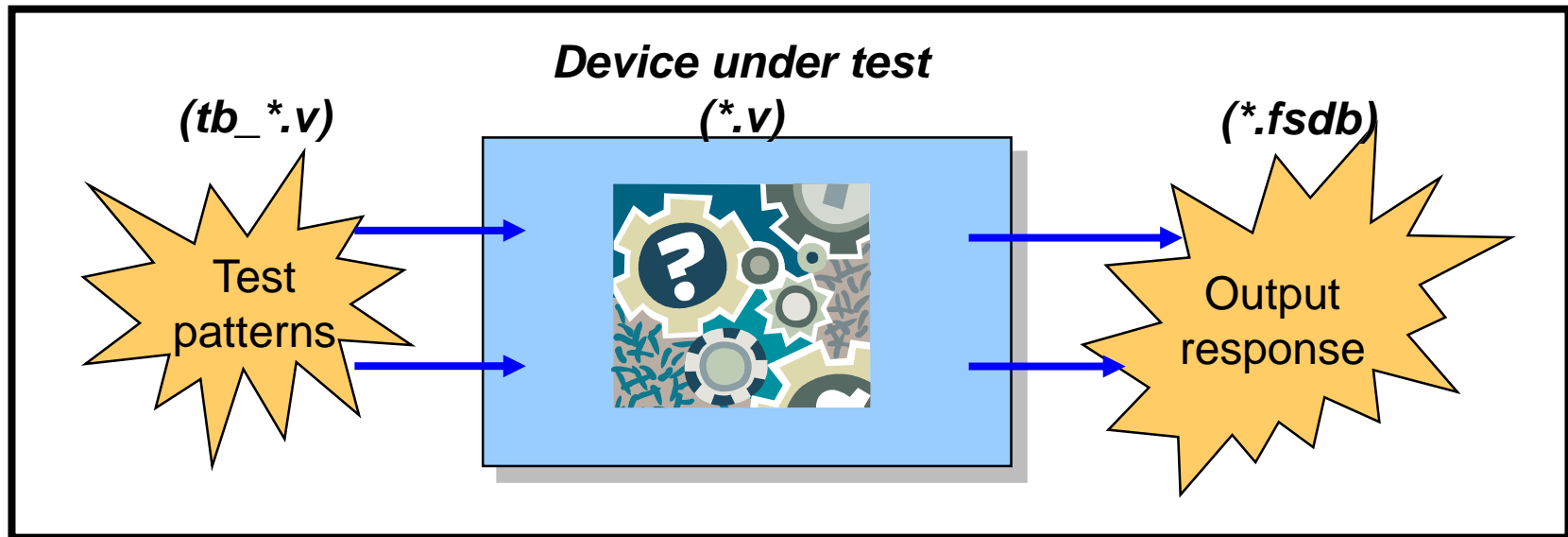





臺灣大學

# Compile and debug (1/2)

- Source

- source /usr/cadence/cshrc
- source /usr/spring\_soft/CIC/verdi.cshrc

- Include the testbench & lib.v files to run simulation

- ncverilog **+access+r** tb\_Comparator\_51.v Comparator\_51.v lib.v



臺灣大學

## Compile and debug (2/2)

```
[r04028@cad39 ~/ICD_HW3]$ ncvcrilög +access+r tb_Comparator_51.v Comparator_51.v lib.v
ncverilog: 10.20-s114: (c) Copyright 1995-2012 Cadence Design Systems, Inc.
file: Comparator_51.v
  module worklib.FAA1:v
    errors: 0, warnings: 0
  module worklib.comparator:v
    errors: 0, warnings: 0
  module worklib.COMPARATOR_51:v
    errors: 0, warnings: 0
    Caching library 'worklib' ..... Done
  Elaborating the design hierarchy:
  Building instance overlay tables:
    $readmemb("in0.dat", i0mem);
```

```
ncsim> run
ncsim: *W,DVEXACC: some objects excluded from $dumpvars
cess to all objects.
      File: ./tb_Comparator_51.v, line = 46, pos
      Scope: tb_51_COMPARATOR
      Time: 0 FS + 0
```


Congratulations! Your score is 70!



臺灣大學
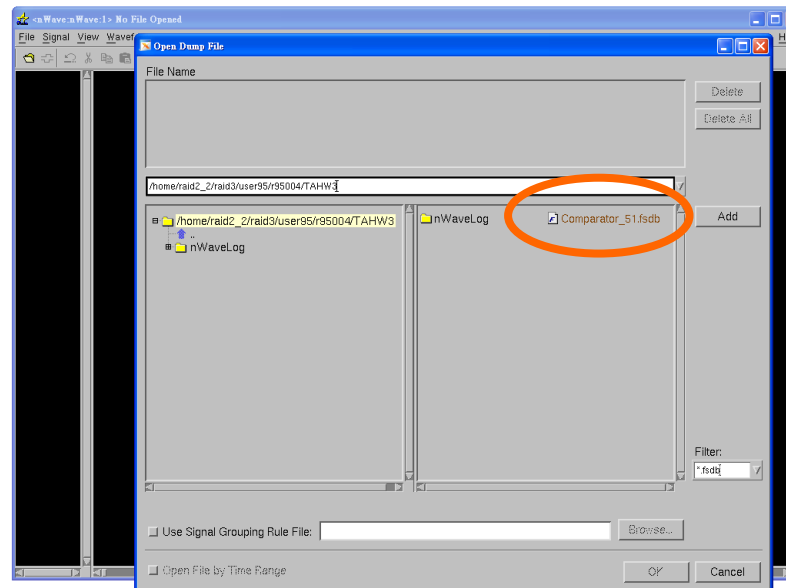
# Execute nWave & Open \*.fsdb


- Execute : *nWave* &
- Open waveform file:
  - File -> Open -> Comparator\_51.fsdb





臺灣大學

# Get signals

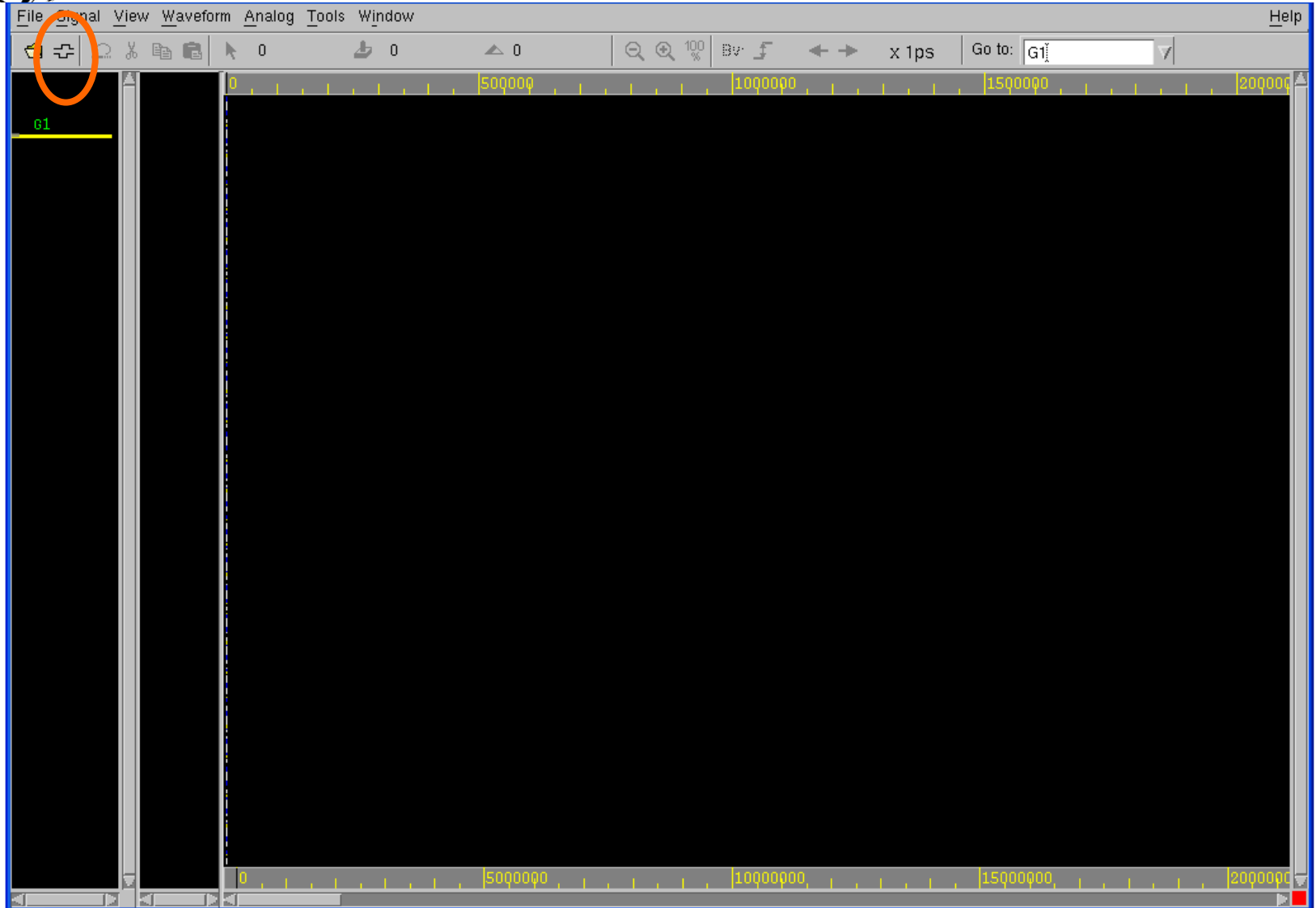



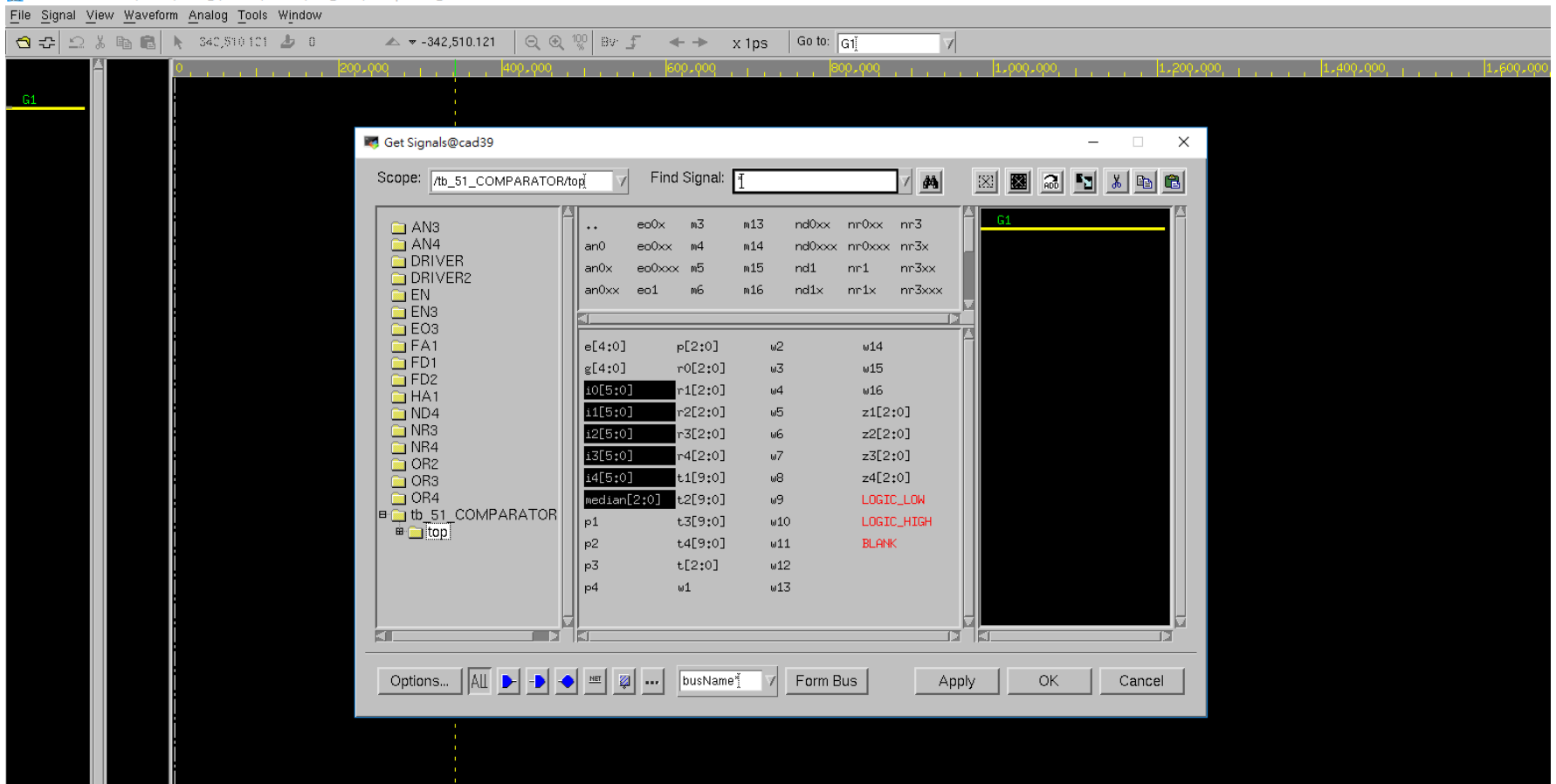
# Find Top Module & Choose signals

臺灣大學


<Novas:nWave:1> /home/raid7\_2/user04/r04028/ICD\_HW3/Comparator\_51.fsd.fsd@cad39





臺灣大學

# Change the radix to be decimal

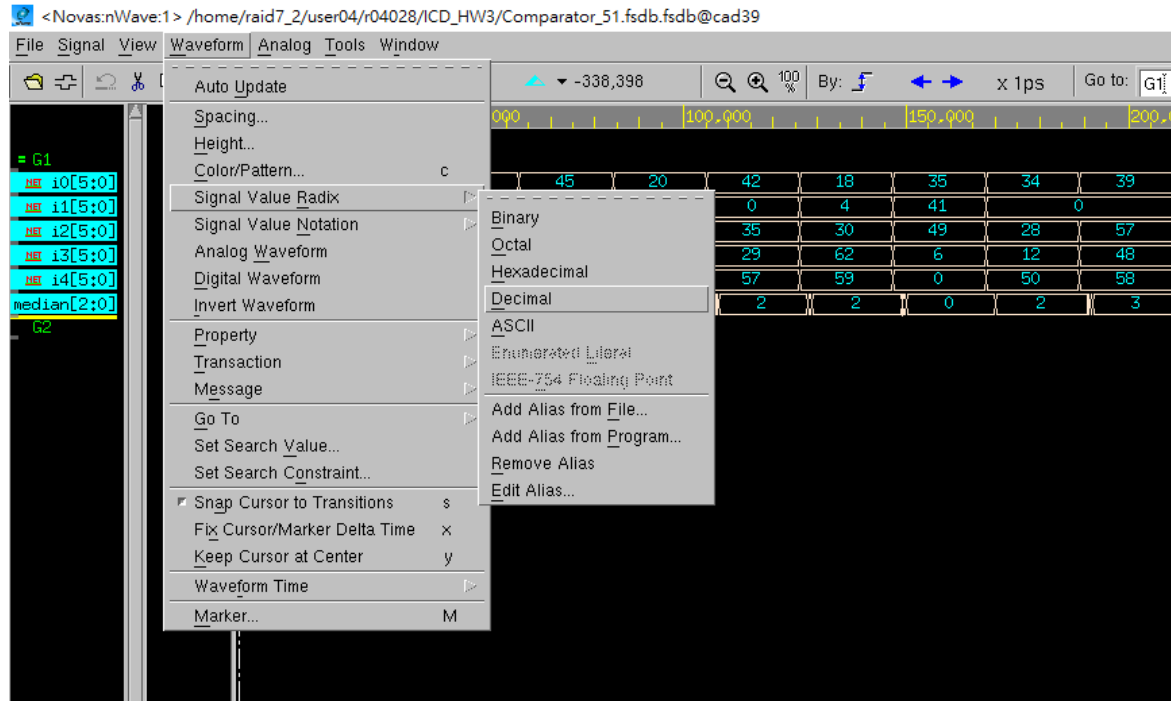

The screenshot shows the Novas.nWave software interface. The 'Signal Value Radix' menu is open, and 'Decimal' is selected. The waveform display shows a table of values for signals i0[5:0], i1[5:0], i2[5:0], i3[5:0], i4[5:0], and median[2:0].

Signal	Value
i0[5:0]	51
i1[5:0]	44
i2[5:0]	29
i3[5:0]	5
i4[5:0]	52
median[2:0]	1



臺灣大學

# Reminder

- Due to 2016/12/16 13:20
- Any further questions, please contact...
  - [r04943028@ntu.edu.tw](mailto:r04943028@ntu.edu.tw)