

# Chapter 10

## Power/Clock Distribution, IO, and Packaging



---

關志達

台灣大學電機系




# Power Distribution

---

- Power Distribution Network functions
  - Carry current from pads to transistors on chip
  - Maintain stable voltage with low noise
  - Provide average and peak power demands
  - Provide current return paths for signals
  - Avoid electromigration & self-heating wearout
  - Consume little chip area and wire
  - Easy to lay out


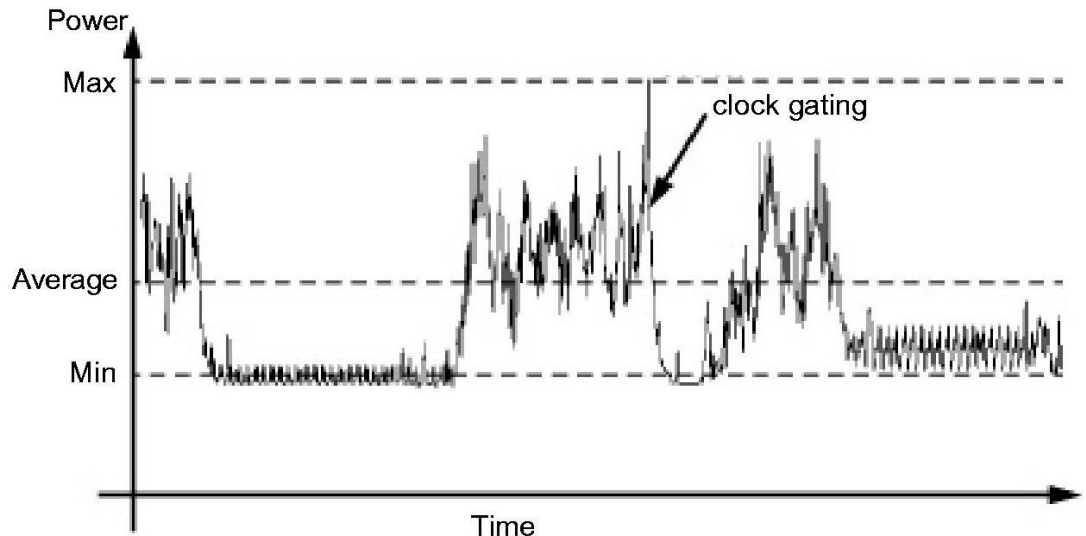
# Power Requirements

- $V_{DD} = V_{DDnominal} - V_{droop}$
- Want  $V_{droop} < +/- 10\%$  of  $V_{DD}$
- Sources of  $V_{droop}$ 
  - IR drops
  - di/dt noise
- $I_{DD}$  changes drastically






# Power Distribution Network

- Network for standard-cell design

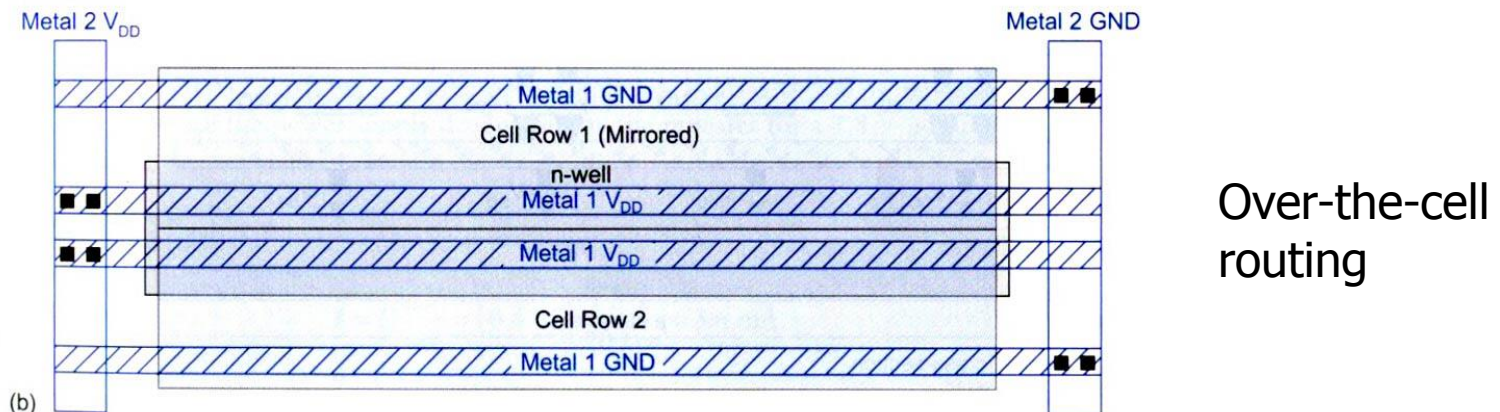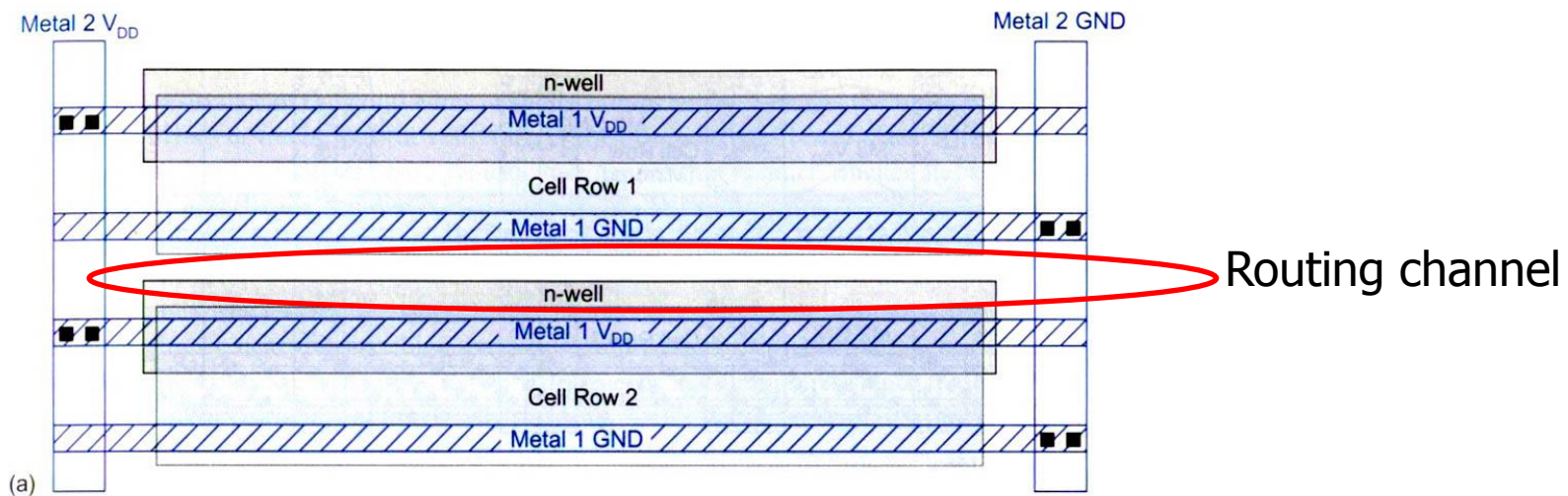
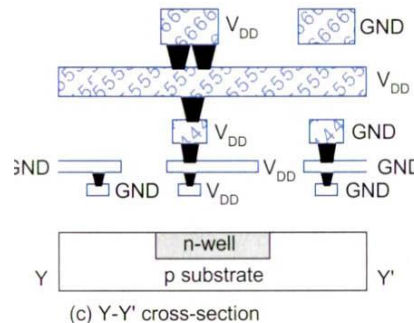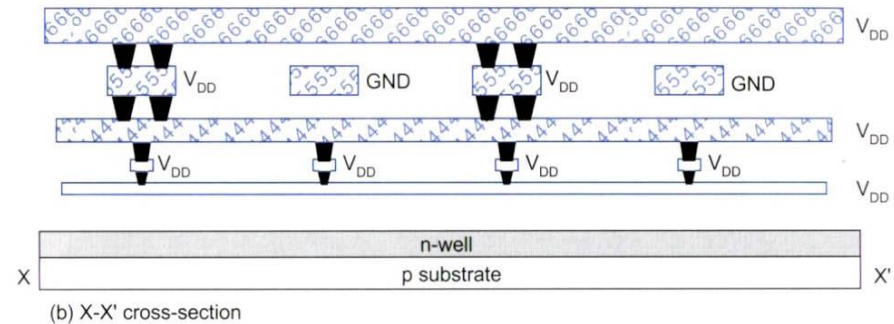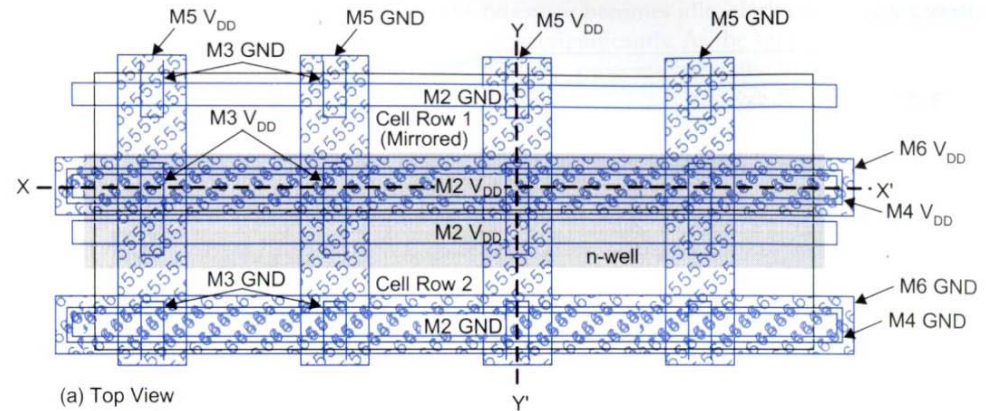
# Power Distribution Network

- Network for high-power IC
  - Use grid of top-level metal to reduce resistance.
  - Plenty of vias to carry large current.





# IR Drop and $Ldi/dt$

---

- IR Drop

- When a large current flow through non-zero-resistance power/ground lines, there will be voltage drop due to Ohm's law.

- $Ldi/dt$  noise


- Wires (especially bonding wires) have inherent inductance and with change of current magnitude along the wires, there will be  $Ldi/dt$  voltage drop across the wires.

- Remedy

- On-chip bypass capacitance can reduce the need to go through long wires for local current needs and thus reduces IR drop and  $Ldi/dt$  effects.

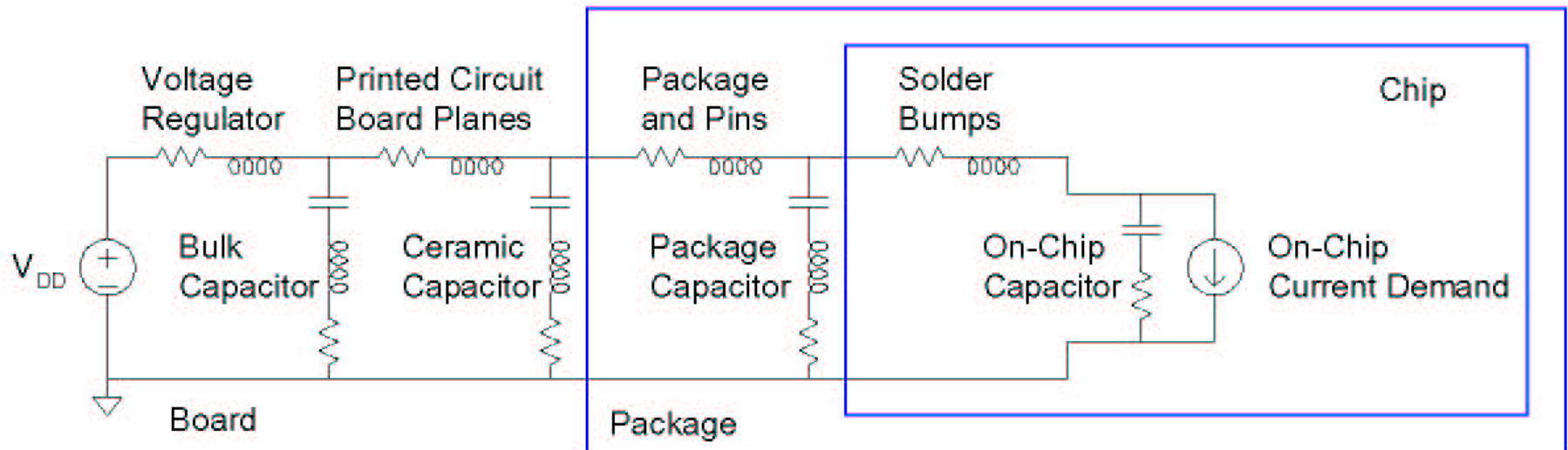
# Power Network Model

- Power comes from regulator on system board
  - Board and package add parasitic R and L
  - Bypass capacitors help stabilize supply voltage
  - But capacitors also have parasitic R and L
- Simulate system for time and frequency responses


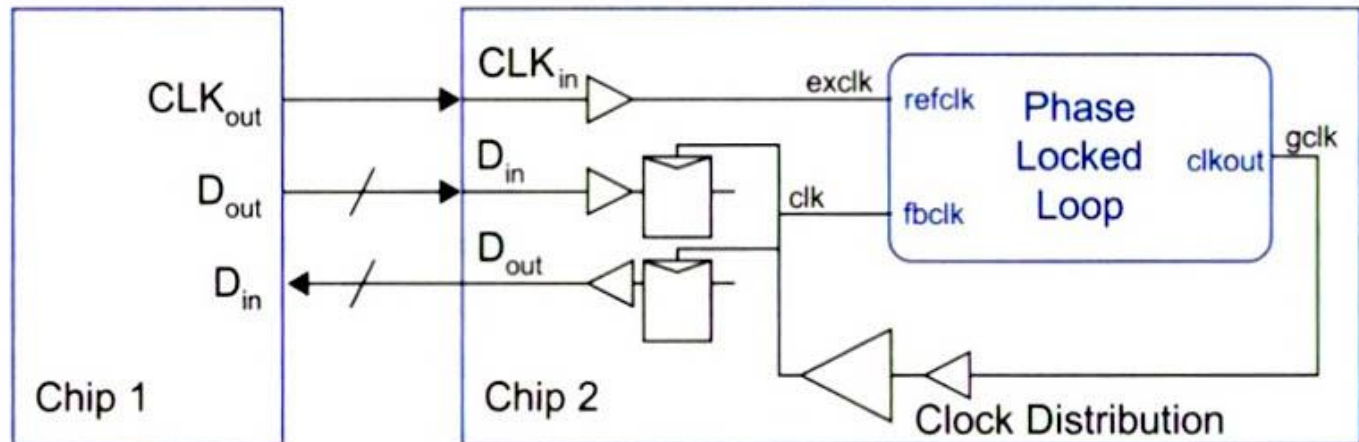
# Clock Generation


- Receive an external clock signal and generate a global clock to be distributed to all sequencing elements and memory.
- Simplest design will be a big buffer.
- Nowadays, many different version/phase/frequency of clock signals are needed in a complicated IC.
- Use PLL to generate clock signals with different phase and frequency.




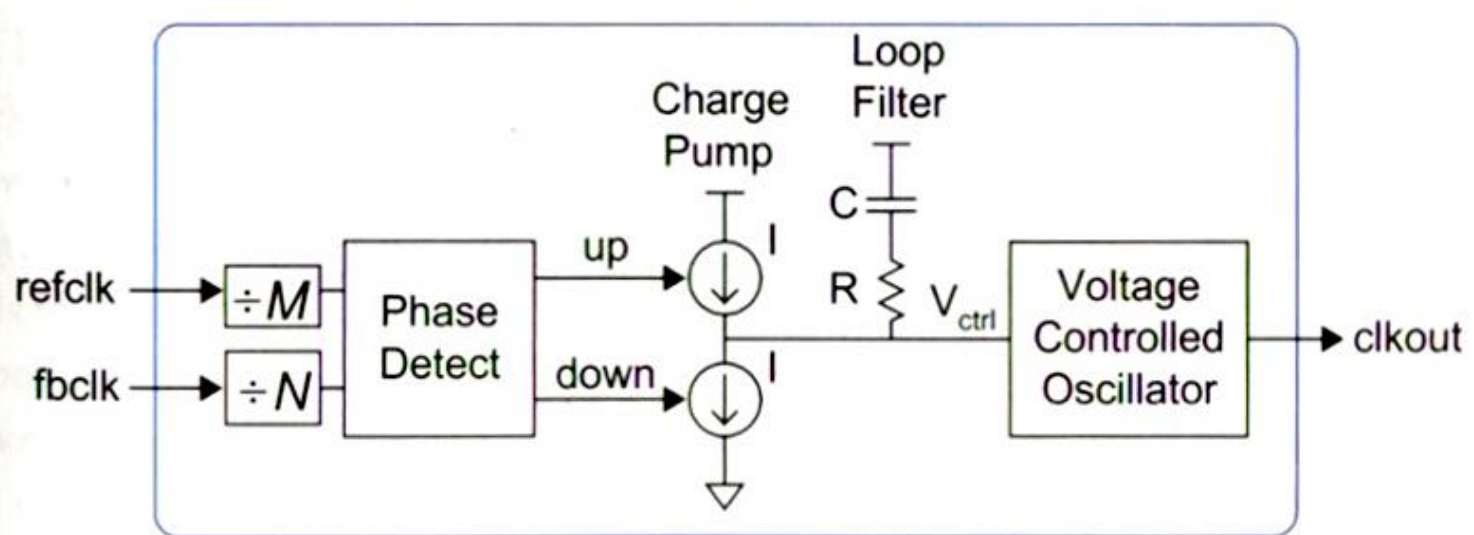
# Phase-Locked Loop

- A phase locked loop (PLL) can be used to synchronize the internal clock of a chip with an external clock. It can also be used to generate an internal clock with higher frequency, especially when the internal clock rate higher than GHz is now common.







# Clock Distribution -- Grid

---

- Use grid on two or more levels to carry clock (similar to power grid)
- Make wires wide to reduce RC delay
- Ensures low skew between nearby points
- But possibly large skew across die

  
# Clock Distribution – H-Tree

- Fractal structure
  - Gets clock arbitrarily close to any point
  - Matched delay along all paths
- Delay variations cause skew
- A and B might see big skew though they are very close. This is due to non-uniform clock loading.


 
# Clock Distribution – Hybrid

- Use H-tree to distribute clock to many points
- Tie these points together with a grid
- Ex: IBM Power4, PowerPC, Alpha
  - H-tree drives 16-64 sector buffers
  - Buffers drive total of 1024 points
  - All points shorted together with grid





# Summary on Clock Signal

---

- Clock is a very sensitive signal. It must be delivered to all registers without distortion in waveform or too much delay skew.
- Clock drivers are needed for driving large load. Actually, drivers are needed to drive all signals with large load, e.g. RESET signal.
- Gated clock is often used to reduce circuit activity and thus power consumption. Make sure that proper gated clock waveform is provided.
- Never use outputs of some complex combinational circuits as clock for some registers (hazard of glitches and spurious switching)



# Chip Inputs/Outputs

---

- Input/Output System functions
  - Communicate between chip and external world
  - Drive large capacitance off chip
  - Operate at compatible voltage levels
  - Provide adequate bandwidth
  - Limit slew rates to control  $di/dt$  noise
  - Protect chip against electrostatic discharge
  - Use small number of pins (low cost)




# I/O Pad Design

---

- Pad types
  - $V_{DD}$  / GND
  - Output
  - Input
  - Bidirectional
  - Analog
 
# Output Pads



- Drive large off-chip loads (2 – 50 pF)
  - With suitable rise/fall times
  - Requires chain of successively larger buffers
- Guard rings to protect against latchup
  - Noise below GND injects charge into substrate
  - Large nMOS output transistor
  - p+ inner guard ring
  - n+ outer guard ring
    - In n-well






  
# Input Pads

- Level conversion
  - Higher or lower off-chip  $V$
  - May need thick oxide gates



 
 
- Noise filtering
  - Schmitt trigger
  - Hysteresis changes  $V_{IH}$ ,  $V_{IL}$



- Protection against electrostatic discharge (ESD, see next page)
  
# ESD Protection

- Static electricity builds up on your body
  - Shock delivered to a chip can fry thin gates
  - Must dissipate this energy in protection circuits before it reaches the gates
- ESD protection circuits
  - Current limiting resistor
  - Diode clamps
- ESD testing
  - Human body model
  - Views human as charged capacitor
  - Voltage source can be 2-4KV or 15KV



- 
- The diagram illustrates a 1T1R1C1 SRAM cell. The top portion shows the cell's connection to a PAD (Peripheral Access Device) through a word line and a bit line. The cell's inputs are En (Enable) and Dout (Data Out), and its output is Din (Data In). The bottom portion provides a detailed view of the 1T1R1C1 core, highlighting the NAND and NOR gates and the access transistors. The core is labeled with En, Dout, and Y (Output).





# Analog Pads

---

- Pass analog voltages directly in or out of chip
  - No buffering
  - Protection circuits must not distort voltages



# MOSIS I/O Pad

  - 1.6  $\mu\text{m}$  two-metal process
  - Protection resistors
  - Protection diodes
  - Guard rings
  - Field oxide clamps



# U. of Utah I/O Pad

 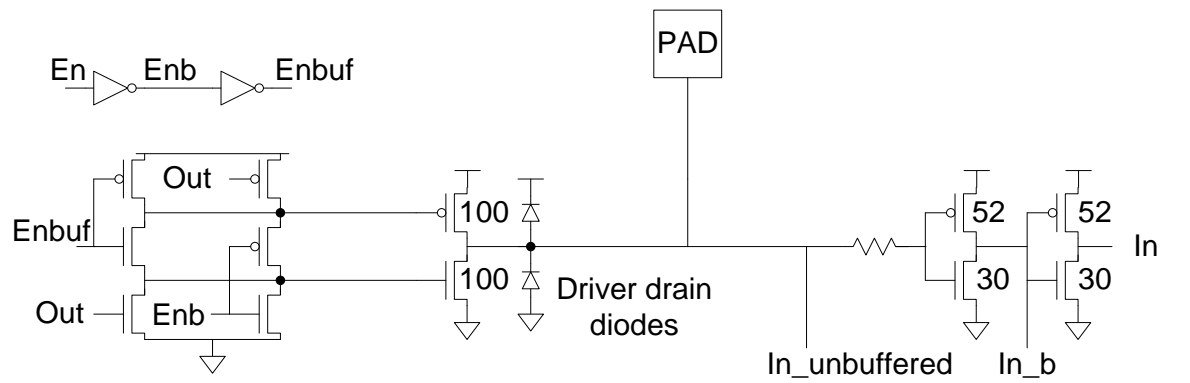- 0.6  $\mu\text{m}$  three-metal process
  - Similar I/O drivers
  - Big driver transistors provide ESD protection
  - Guard rings around driver






# Packages

---

- Package functions
  - Electrical connection of signals and power from chip to board
  - Little delay or distortion
  - Mechanical connection of chip to board
  - Removes heat produced on chip
  - Protects chip from mechanical damage
  - Compatible with thermal expansion
  - Inexpensive to manufacture and test

# Package Types

- Through-hole vs. surface mount

 



# Multi-chip Modules (MCM)

- a. k. a. System in Package (SiP)
- Pentium Pro MCM
  - Fast connection of CPU to cache
  - Expensive, requires known good dice

