

Chapter 9


Memories (Array Subsystems)



關志達

台灣大學電機系

Categories of Memory Arrays

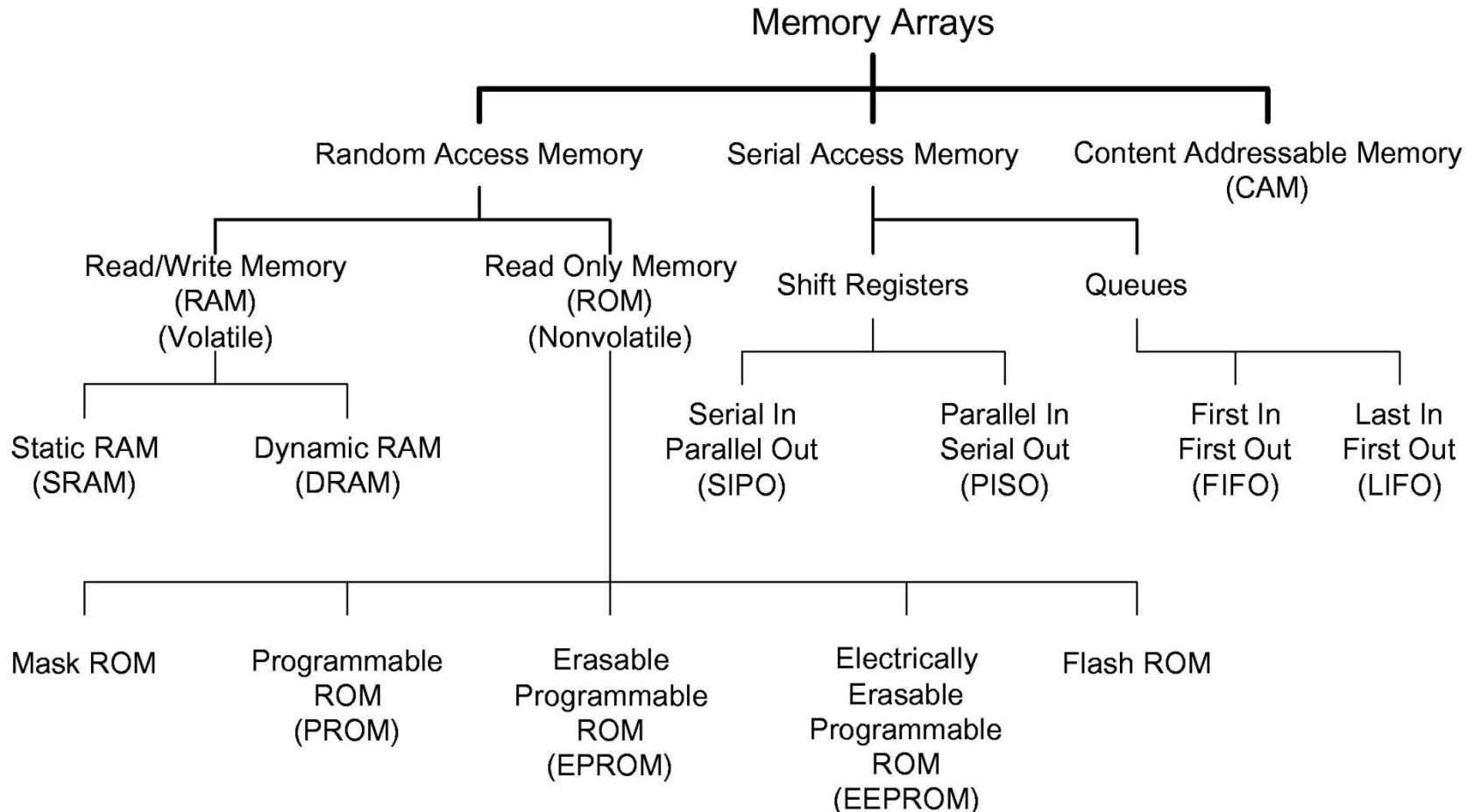




Introduction

- Category of random access memory
 - ROM (read-only memory)
 - Nonvolatile
 - Mask ROM, EPROM, EEPROM, Flash (variant of EEPROM, erases entire blocks rather than individual bits)
 - RAM (read/write memory)
 - Volatile
 - Static vs. dynamic structures
 - Area, speed, leakage, cost tradeoff
- Memory cells can have one or more ports for access

Array Architecture

 
- 2^n words of 2^m bits each
- If $n \gg m$, fold by 2^k into fewer rows of more columns



- Good regularity - easy to design
- Very high density if good cells are used



6T SRAM Cell

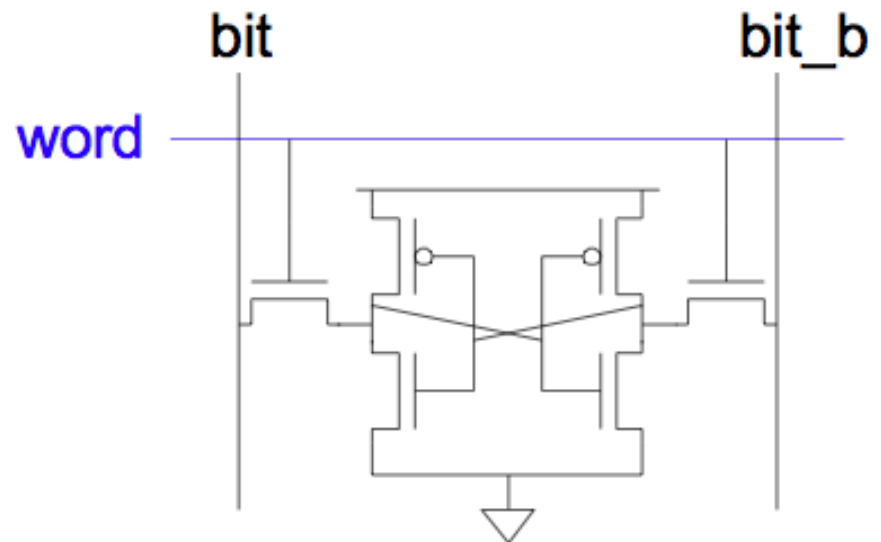- Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- Read
 - Precharge bit, bit_b
 - Raise wordline
- Write
 - Drive data onto bit, bit_b
 - Raise wordline





SRAM Read

 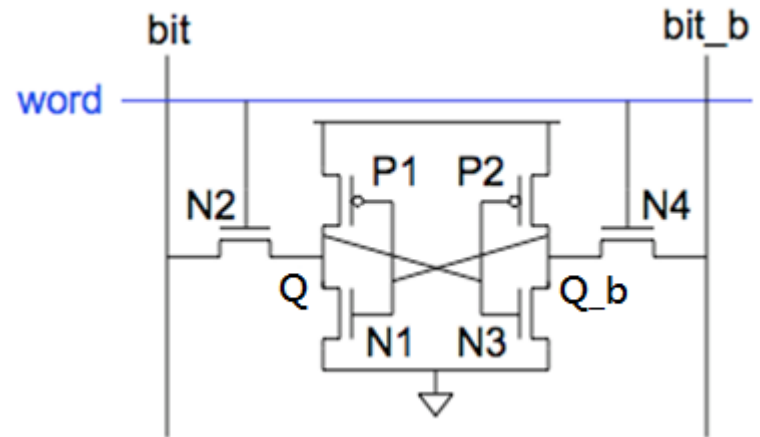- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex: $Q=0$, $Q_b=1$
 - bit discharges, bit_b stays high
 - But Q bumps up slightly
- Read stability
 - Q must not flip
 - $N1 \gg N2$




SRAM Write

 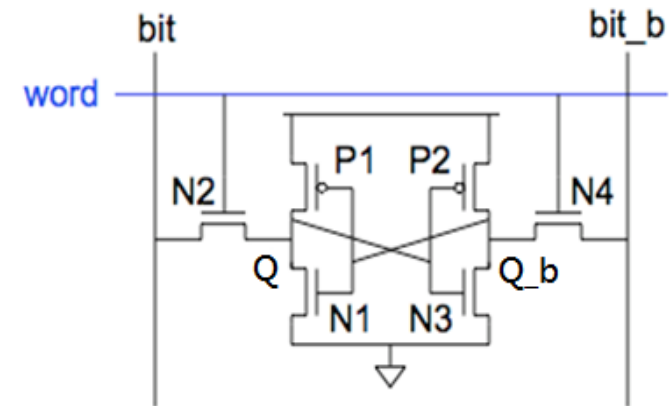- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex: $Q=0$, $Q_b=1$, $\text{bit}=1$, $\text{bit}_b=0$
 - Force Q_b low, then Q rises high
- Writability
 - Must overpower feedback inverter
 - $N2 \gg P1$




SRAM Sizing

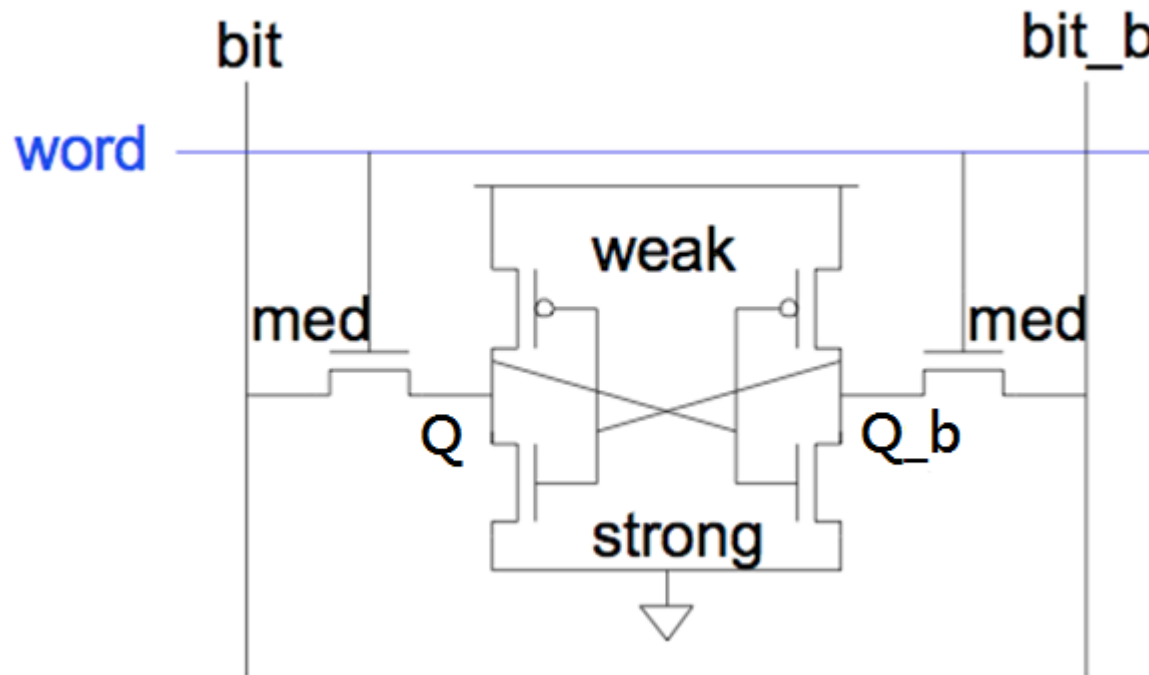- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell





SRAM Column Example

Read

 


Write

 
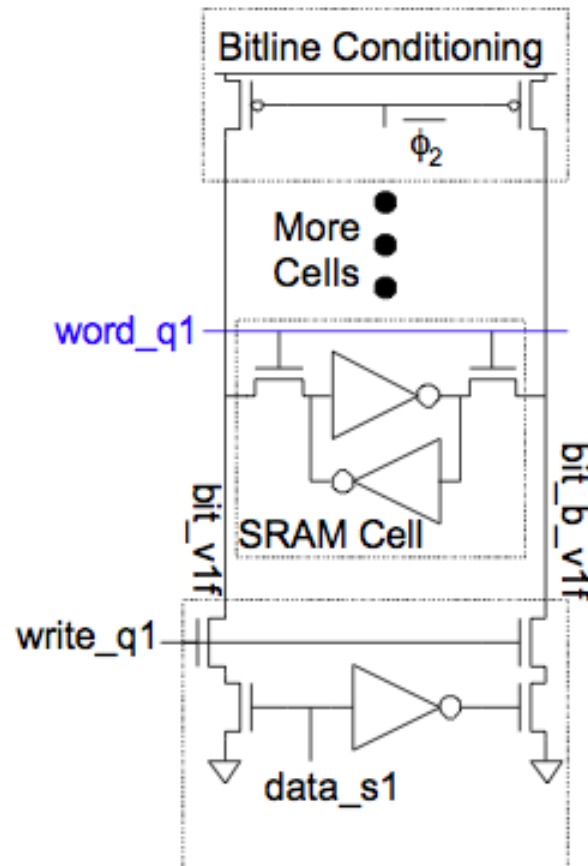


Decoders

 
- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates



static CMOS

  


pseudo nMOS

 


Large Decoders

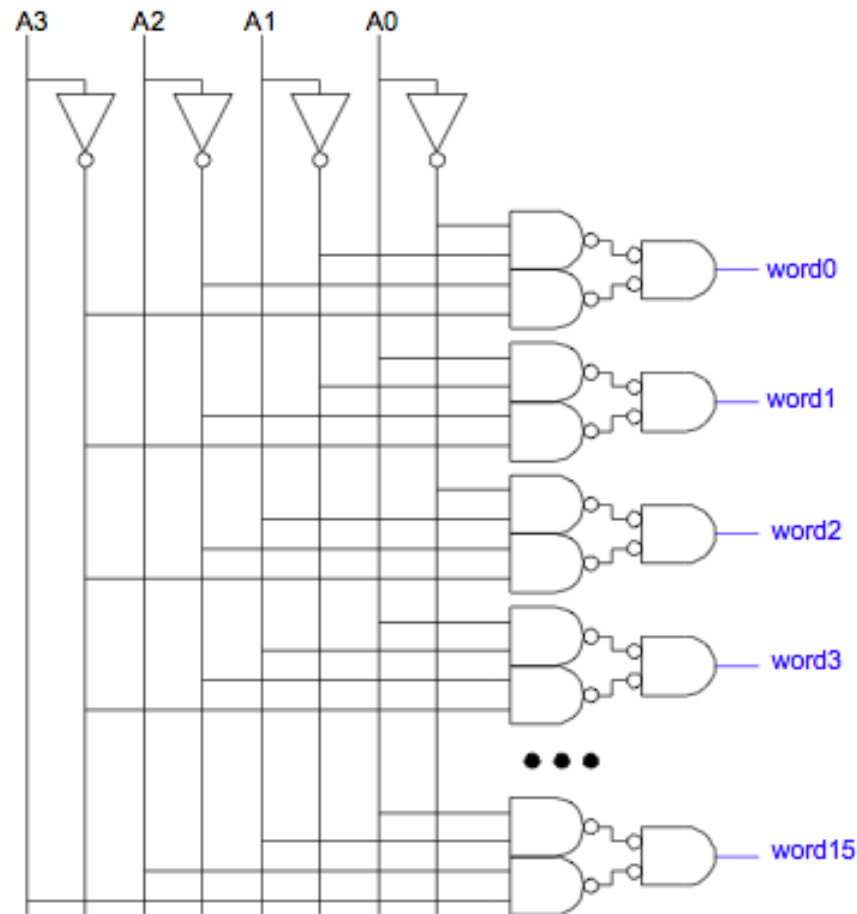- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

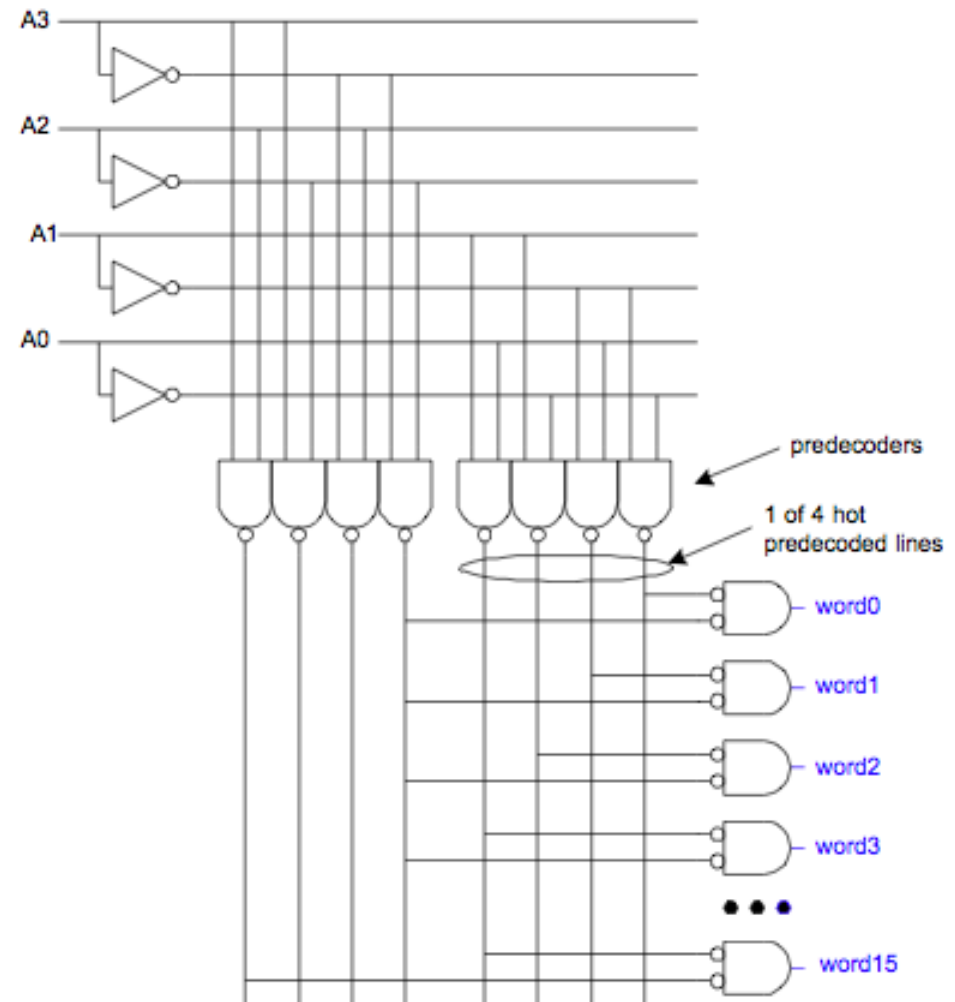- Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area






Column Circuitry


- Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing

Bitline Conditioning

- Precharge bitlines high before reads

 

 - Equalize bitlines to minimize voltage difference and thus ensure correct sensing using sense amplifiers






Sense Amplifiers


- Bitlines have many cells attached
 - Ex: 64-kbit SRAM has 256 rows x 256 cols
 - 256 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- Sense amplifiers are triggered on small voltage swing (reduce ΔV)

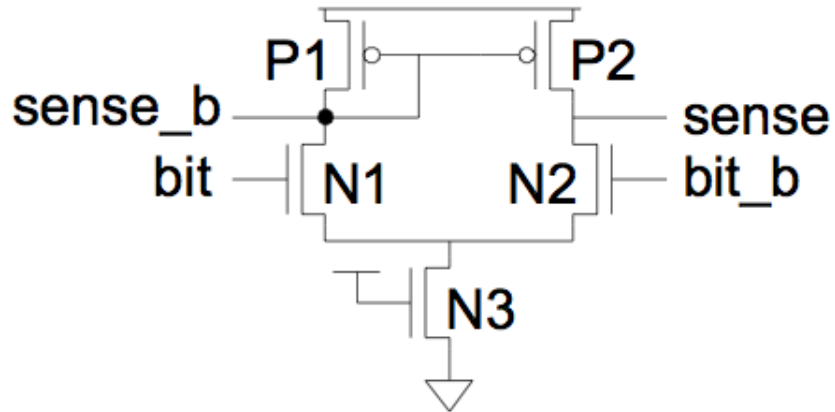- Differential pair requires no clock
- But always dissipates static power



Clocked Sense Amp

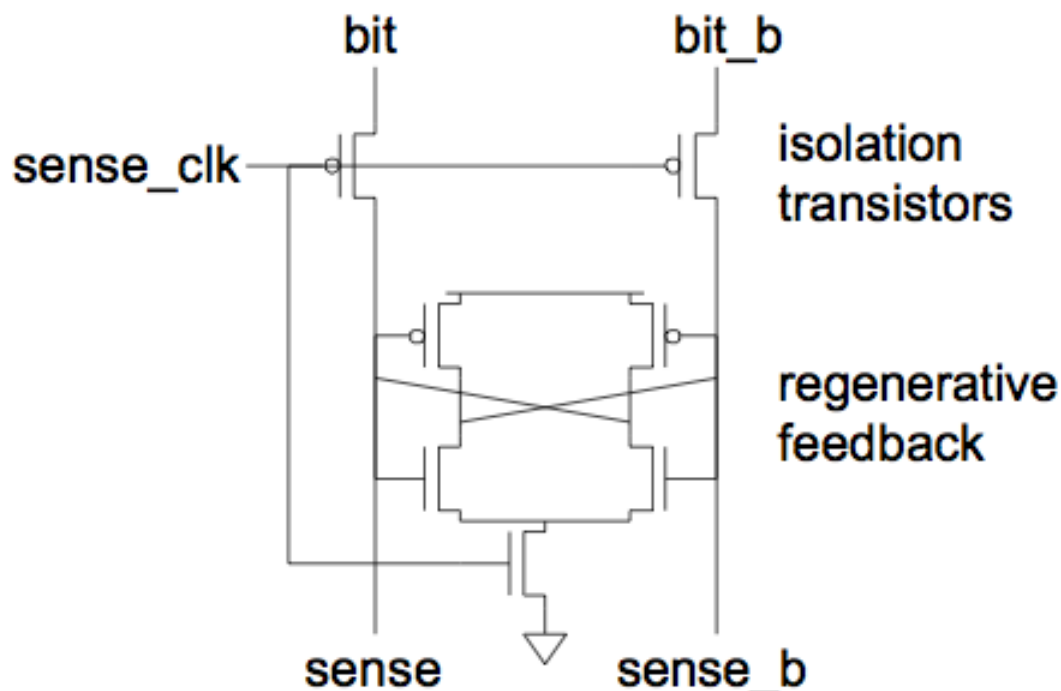- Clocked sense amp saves power
- Requires sense_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance during sensing






Column Multiplexing

- Recall that array maybe folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers


Tree Decoder MUX

 - Column mux can use pass transistors
 - Use NMOS only
- One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed



Single Pass-Gate MUX

 - Eliminate series transistors with separate decoder to do the binary-unary decoding.






Multiple Ports

- We have considered single-ported SRAM
 - One read or one write on each cycle
- Multiported SRAM are needed for register files
- Examples:
 - Pipelined processor must read two sources and write a third result each cycle
 - Superscalar processor must read and write many sources and results each cycle

Dual-Ported SRAM

 
- Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write



- Do two reads and one write by time multiplexing
 - Read during $\phi 1$, write during $\phi 2$


Multi-Ported SRAM

 - Add more access transistors hurts read stability
- Multiported SRAM isolates reads from state nodes
- Single-ended design minimizes number of bitlines



Future Trend


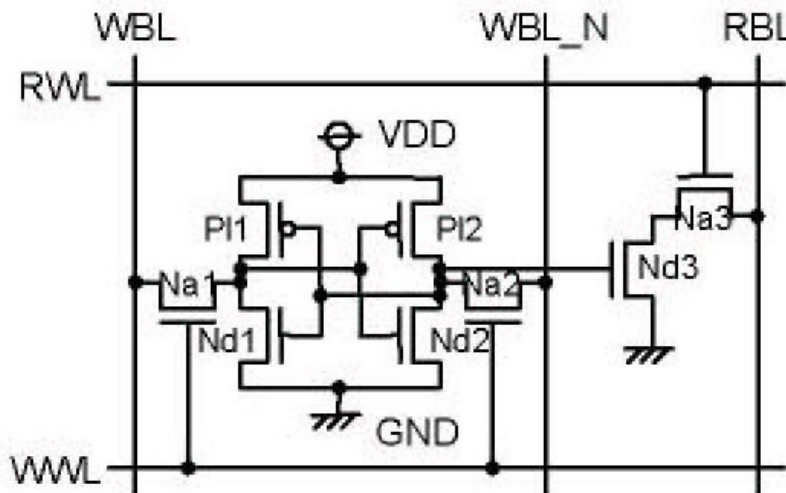
- Use 8T SRAM cell in 65nm-32nm technology
 - Morita VLSI Circuits Symp. 2007.
 - Separate read port from write port
 - Can support Vdd down to 0.42V



- [illegible]

DRAM

  - Trench capacitor can drastically decrease the cell area
- Schematic and scanning electron microscope (SEM) photo.






Read-Only Memories

- Read-only memories are nonvolatile
 - Retain their contents when power is removed
- Mask-programmed ROMs use one transistor per bit
 - Presence or absence determines 1 or 0

ROM Example

- 4-word x 6-bit ROM

- Represented with dot diagram
- Dots indicate 1's in ROM

 


Word 0: **010101**

Word 1: **011001**

Word 2: **100101**




Word 3: **101010**

 

Looks like 6 4-input pseudo-nMOS NORs

NAND ROMs

 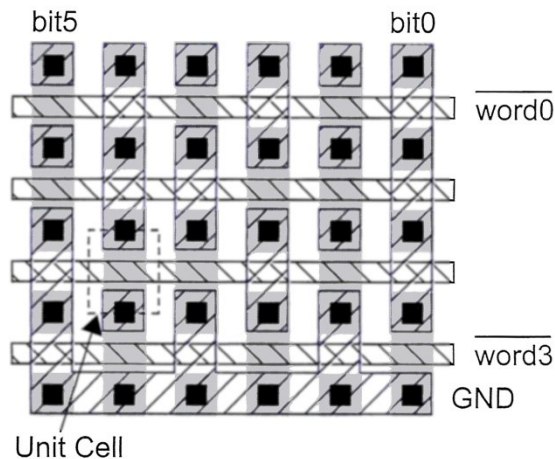 - Smaller area due to no ground lines.
- Cell area can be further reduced by eliminating the contacts and using an extra implant step that makes the V_{th} negative and turns on the transistor permanently.




PROMs and EPROMs

■ Programmable ROMs

- Build array with pull-down transistors at every site
- Burn out fuses to disable unwanted transistors; one-time programmable (OTP).

■ Erasable Programmable ROMs

 - Use floating gate to turn off unwanted transistors
- Negative charges are drawn into the isolated floating gate, which effectively increases the threshold voltage and turns off the transistor.
- EPROM, EEPROM, Flash






Serial Access Memories

- Serial access memories do not use an address
 - Shift registers
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Queues (FIFO, LIFO)


Shift Register

 - Shift register store and delay data
- Simple design: cascade of registers
 - Watch your hold times, i.e., the signal may travel too fast.




Dense Shift Registers

 - Flip-flops are not very area-efficient
- For large shift registers, keep data in SRAM instead
- Move read/write pointers to RAM rather than data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle
 - Can use ring counters to replace counters and address decoders




Serial In Parallel Out

 - 1-bit shift register reads in serial data
 - After N steps, presents N-bit parallel output




Parallel In Serial Out

 - Load all N bits in parallel when shift=0
 - Then shift one bit out per cycle



Queues

 - Queues allow data to be read and written at different rates
- Read and write each use their own clock and data
- Queue indicates whether it is full or empty
- Build with SRAM and read/write counters (pointers)







FIFO, LIFO Queues

- First In First Out (FIFO)
 - Initialize read and write pointers to first element
 - Queue is EMPTY
 - On write, increment write pointer
 - If write almost catches read, Queue is FULL
 - On read, increment read pointer
- Last In First Out (LIFO)
 - Also called a stack
 - Use a single stack pointer for read and write


Content Addressable Memory

  - Read and write memory as usual
- A content addressable memory takes in a data word and compare it with stored words and generates a match signal, which can be used to address a RAM. This is how the translation look-aside buffer works in a cache.



10-T CAM Cell

 - Add four match transistors to 6T SRAM
- Match line will be pulled low when 'cell' and 'bit' mismatch.



CAM Cell Operation


- Read and write like ordinary SRAM

- For matching:

- Leave wordline low
- Precharge matchlines
- Place key on bitlines
- Matchlines evaluate

- Miss line

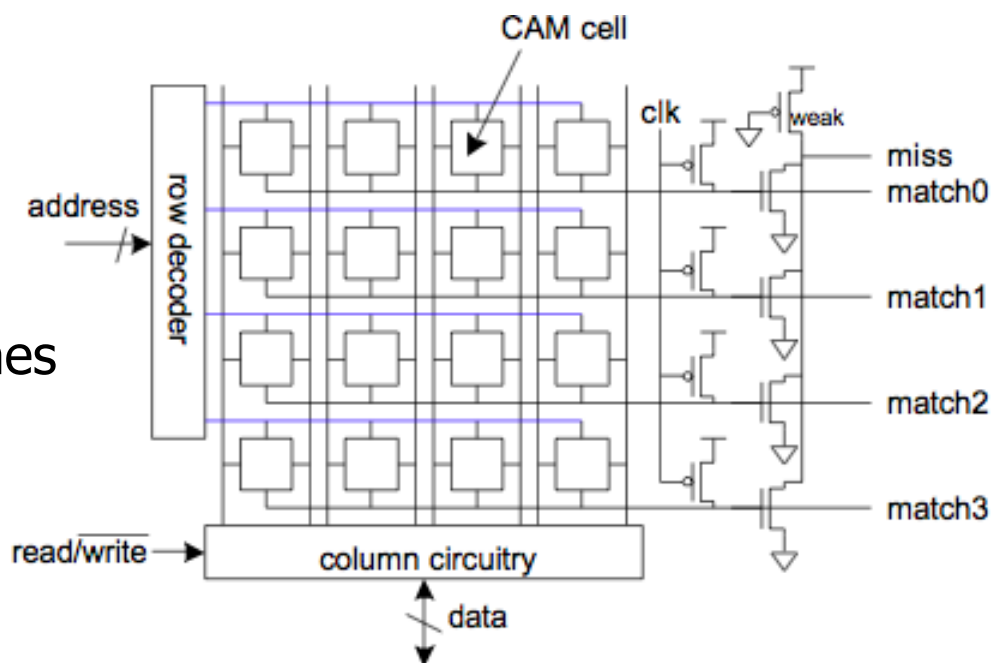- Pseudo-nMOS NOR match lines
- Goes high if no words match




PLAs

- A Programmable Logic Array performs any function in sum-of-products form
- Literals: inputs & complements
- Products/Minterms: AND of literals
- Outputs: OR of Minterms
- Example: Full Adder



$$s = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}\bar{c} + abc$$

$$c_{out} = ab + bc + ac$$

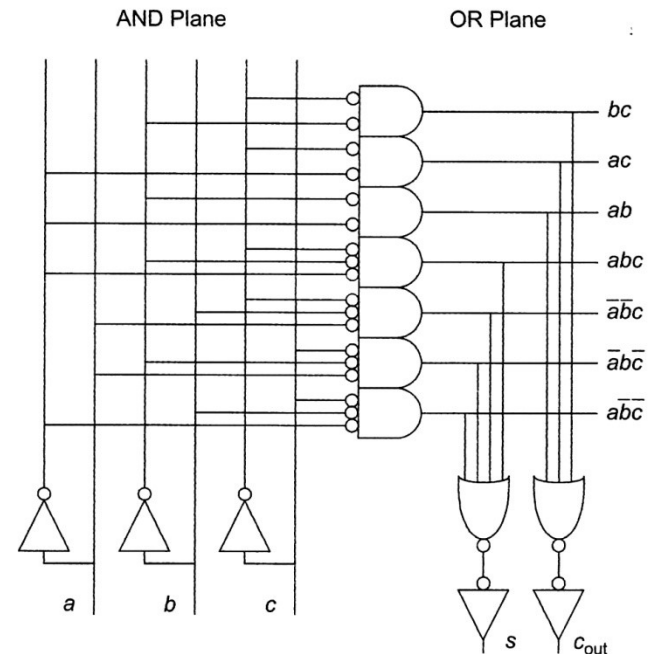


NOR-NOR PLAs

 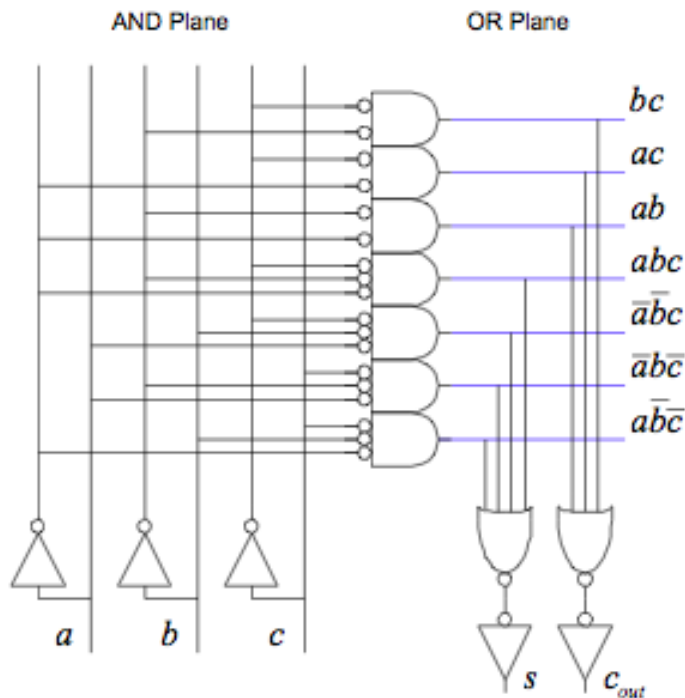- ANDs and ORs are not very efficient in CMOS
- Dynamic or Pseudo-nMOS NORs are very efficient
- Use DeMorgan's Law to convert to all NORs



PLA Schematic

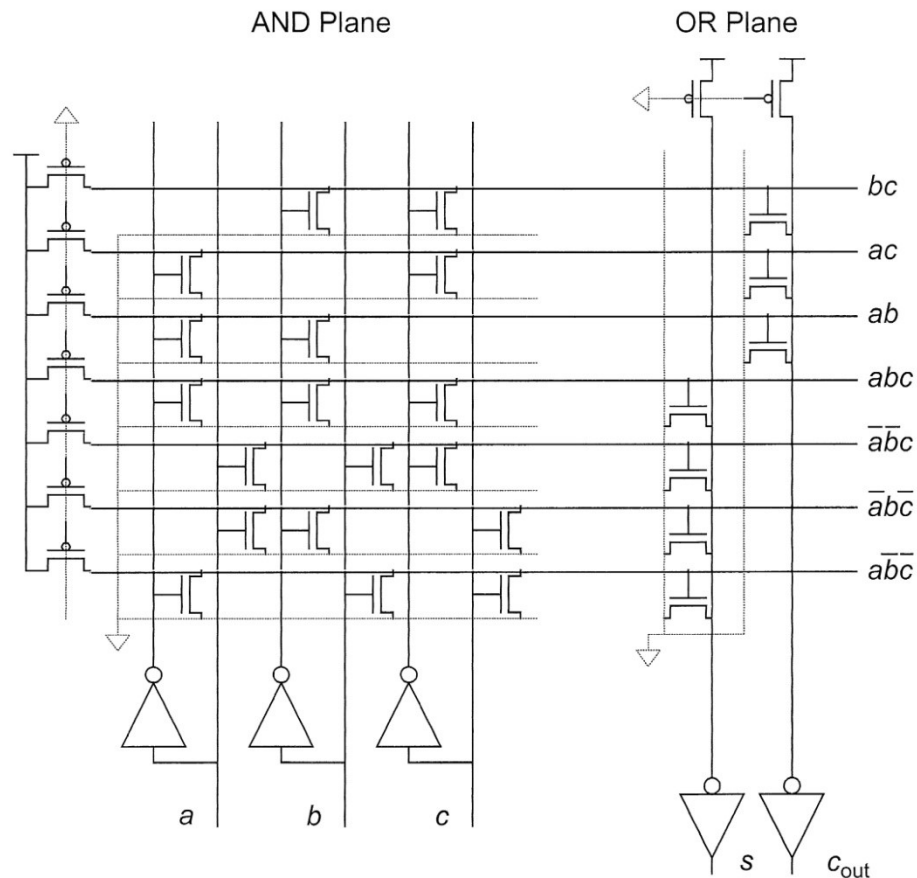- Pseudo-NMOS version
- Dynamic and self-timed version can be faster.





PLAs vs. ROMs

- The OR plane of the PLA is like the ROM array
- The AND plane of the PLA is like the ROM decoder
- PLAs are more flexible than ROMs
 - No need to have 2^n rows for n inputs
 - Only generate the minterms that are needed
 - Take advantage of logic simplification